



Zeal Education Society's
ZEAL POLYTECHNIC, PUNE.

NARHE | PUNE -41 | INDIA

SECOND YEAR (SY)

DIPLOMA IN ELECTRICAL ENGINEERING

SCHEME: I

SEMESTER: IV

**NAME OF SUBJECT: DIGITAL ELECTRONICS AND
MICROCONTROLLER**

SUBJECT CODE: 22421

MSBTE QUESTION PAPERS & MODEL ANSWERS

1. MSBTE SUMMER-19 EXAMINATION

2. MSBTE WINTER-19 EXAMINATION

22421

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

5 × 2 = 10

- (a) Construct OR gate using NAND gate.
- (b) Compare Harrod and Non-Neuman architecture. (any two points)
- (c) Write the excitation table for T-FF.
- (d) Define : (i) Address bus (ii) Data bus.
- (e) List the different addressing modes of 8051.
- (f) Define : (i) Assembler (ii) Compiler
- (g) Find the number of address lines required for
 - (i) 4K RAM (ii) 8K ROM

2. Attempt any THREE of the following :

3 × 4 = 12

- (a) State & explain De-Morgan's first theorem.
- (b) Compare microprocessor & microcontroller. (any four points)
- (c) Solve the following SOP expressions with the help of K-map :
 - (i) $F(A, B, C, D) = \sum m(0, 1, 3, 4, 5, 7)$
 - (ii) $F(A, B, C) = \sum m(0, 1, 4, 5, 6, 7)$
- (d) Write any two laws of Boolean algebra. Justify with the help of truth table.

- 3. Attempt any THREE of the following :** **12**
- (a) List any eight features of microcontroller 8051.
 - (b) Compare TTL, CMOS & ECL families on the following :
 - (i) Power dissipation
 - (ii) Noise Margin
 - (iii) Speed of Operation
 - (iv) Fan-in
 - (c) Describe the function of following pins of 8051 :
 - (i) $\overline{\text{PSEN}}$
 - (ii) RESET
 - (iii) ALE
 - (iv) $\overline{\text{EA}}$
 - (d) Draw logic diagram of 4 : 1 multiplexer & give it's truth table.
- 4. Attempt any THREE of the following :** **12**
- (a) Draw a neat labelled interfacing diagram of 8051 with stepper motor.
 - (b) Implement OR gate using transistor.
 - (c) Write the alternative function of Port-3 pins.
 - (d) Draw master-slave JK FF & write it's truth table.
 - (e) Explain Boolean processor of 8051.
- 5. Attempt any TWO of the following :** **12**
- (a) Execute the following program & specify the contents of Accumulator & status of PSW after execution. Also draw the format of PSW
MoV A, #0FH
MoV B, #03H
Div AB
End
 - (b) Develop an ALP to generate square wave of 1kHz at port pin P1.3. Draw flowchart for it.
 - (c) Explain full adder with it's logic diagram & truth table.

6. Attempt any TWO of the following :**12**

- (a) Construct 3-bit synchronous UP counter using flipflop. Also draw it's timing diagram.
 - (b) Describe the following assembler directives with one example of each :
 - (i) ORG
 - (ii) DB
 - (iii) EQU
 - (iv) END
 - (v) CODE
 - (vi) DATA
 - (c) Develop an ALP for interfacing of LED's with Port 1 of 8051. Draw interfacing diagram for the same.
-



SUMMER– 2019 Examinations

Subject Code: 22421


Model Answer

Page 1 of 13

Important suggestions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance. (Not applicable for subject English and communication skills)
- 4) While assessing figures, examiner may give credit for principle components indicated in a figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case some questions credit may be given by judgment on part of examiner of relevant answer based on candidate understands.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q.1	Attempt any FIVE of the following	5x2= 10 Marks												
	a) Construct OR gate using NAND gate.													
Ans:	<p>OR gate using NAND gate:</p> <div style="text-align: center;"> </div> <p style="text-align: right;">or equivalent</p>	(2 Marks)												
	b) Compare Harward and Von-Neuman architecture. (any two points)													
Ans:	(Any Two point expected: 1 Mark each, Total 2 Marks)													
	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;">S.No</th> <th style="width: 45%;">Harward architecture</th> <th style="width: 45%;">Von-Neumann architecture</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">1</td> <td>The computer has two separate memories for storing data and program. e.g. 8051 microcontroller</td> <td>The computer has single storage system(memory) for storing data as well as program to be executed e.g. 8085 microprocessor</td> </tr> <tr> <td style="text-align: center;">2</td> <td>Faster Execution of program</td> <td>Slower execution of program</td> </tr> <tr> <td style="text-align: center;">3</td> <td>Requires more hardware because of separate bus-structure</td> <td>Requires less hardware because of single bus structure</td> </tr> </tbody> </table>	S.No	Harward architecture	Von-Neumann architecture	1	The computer has two separate memories for storing data and program. e.g. 8051 microcontroller	The computer has single storage system(memory) for storing data as well as program to be executed e.g. 8085 microprocessor	2	Faster Execution of program	Slower execution of program	3	Requires more hardware because of separate bus-structure	Requires less hardware because of single bus structure	
S.No	Harward architecture	Von-Neumann architecture												
1	The computer has two separate memories for storing data and program. e.g. 8051 microcontroller	The computer has single storage system(memory) for storing data as well as program to be executed e.g. 8085 microprocessor												
2	Faster Execution of program	Slower execution of program												
3	Requires more hardware because of separate bus-structure	Requires less hardware because of single bus structure												

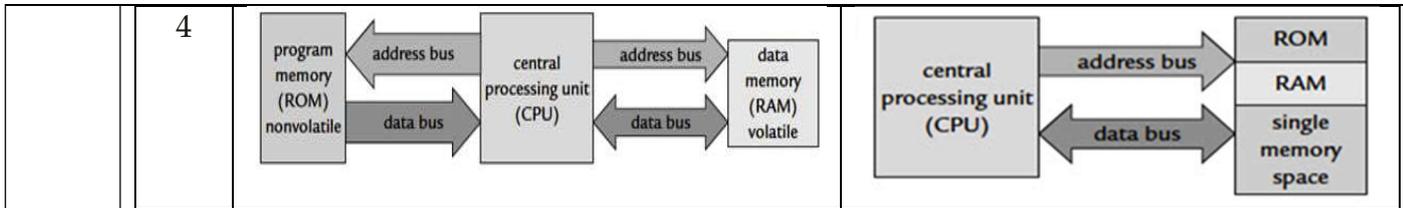

c) Write the excitation table for T-FF.

Ans: **Excitation table for T-FF: (2 Marks)**

$Q(t)$	$Q(t+1)$	T	Operation
0	0	0	No change
0	1	1	Complement
1	0	1	Complement
1	1	0	No Change

d) Define : (i) Address bus (ii) Data bus.

Ans: **Address bus: (1 Mark)**

It is the bunch of wires which carry binary address of the peripheral that is connected to CPU

Data Bus: (1 Mark)

It is the bunch of wires which carry binary data that is exchanged between CPU and peripheral

e) List the different addressing modes of 8051.

Ans: **Following addressing modes of 8051: (Any Two point expected: 1 mark each, Total 2 Mark)**

- 1) Immediate addressing mode
- 2) Direct Addressing mode
- 3) Register addressing mode
- 4) Register indirect addressing mode
- 5) Indexed addressing mode

f) Define : (i) Assembler (ii) Compiler

Ans: **(i) Assembler: (1 Mark)**

Assembler converts assembly language program into object code or machine code

(ii) Compiler: (1 Mark)

Compiler converts higher level language programs (C language) into machine codes



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION
(Autonomous)
(ISO/IEC-27001-2005 Certified)

SUMMER– 2019 Examinations

Subject Code: 22421

Model Answer


Page 3 of 13

g)	Find the number of address lines required for (i) 4K RAM (ii) 8K ROM																									
Ans:	(i) For 4K RAM : - 12 address line as $2^{12}=4096$	(1 Mark)																								
	(ii) For 8K ROM : - 13 address lines as $2^{13}=8192$	(1 Mark)																								
Q. 2	Attempt any THREE of the following	3x4= 12 Marks																								
a)	State & explain De-Morgan's first theorem.																									
Ans:	De-Morgan's first theorem:	(4 Marks)																								
	<p style="text-align: center;">DeMorgan's Theorem is mainly used to solve the various Boolean algebra expressions. The Demorgan's theorem defines the uniformity between the gate with same inverted input and output. It is used for implementing the basic gate operation likes NAND gate and NOR gate.</p> <p style="text-align: center;">It states that “when OR sum of two variables is inverted, it is equivalent to ANDing of NOT output of each variable”</p> $\overline{A + B} = \overline{A} . \overline{B}$																									
b)	Compare microprocessor & microcontroller. (any four points)																									
	(Any four point expected: 1 mark each, total 4 Mark)																									
Ans:	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;">S.No</th> <th style="width: 45%;">Microprocessor</th> <th style="width: 45%;">Microcontroller</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">1</td> <td>It is just a CPU i.e. central processing unit with address and data bus. It requires memory and other peripherals to make a computer</td> <td>It is a computer on single chip. It consists of CPU memory and peripherals in a single chip.</td> </tr> <tr> <td style="text-align: center;">2</td> <td>It does not have digital input output ports. Needs to be externally connected</td> <td>It has several digital input output lines 8051 has 32 I/O lines</td> </tr> <tr> <td style="text-align: center;">3</td> <td>It is mainly used for information processing, multimedia and for making desktop computer.</td> <td>It is mainly used for digital control in industrial applications or in home appliances</td> </tr> <tr> <td style="text-align: center;">4</td> <td>It can have large external memory</td> <td>Memory capacity is small</td> </tr> <tr> <td style="text-align: center;">5</td> <td>It is based on VonNeumann architecture</td> <td>It is based on Harward architecture</td> </tr> <tr> <td style="text-align: center;">6</td> <td>Cost and size of hardware is large</td> <td>It is cheaper in cost and compact in size</td> </tr> <tr> <td style="text-align: center;">7</td> <td>Example: 8085 microprocessor, Pentium processor</td> <td>Example: 8051, 8052 microcontroller</td> </tr> </tbody> </table>		S.No	Microprocessor	Microcontroller	1	It is just a CPU i.e. central processing unit with address and data bus. It requires memory and other peripherals to make a computer	It is a computer on single chip. It consists of CPU memory and peripherals in a single chip.	2	It does not have digital input output ports. Needs to be externally connected	It has several digital input output lines 8051 has 32 I/O lines	3	It is mainly used for information processing, multimedia and for making desktop computer.	It is mainly used for digital control in industrial applications or in home appliances	4	It can have large external memory	Memory capacity is small	5	It is based on VonNeumann architecture	It is based on Harward architecture	6	Cost and size of hardware is large	It is cheaper in cost and compact in size	7	Example: 8085 microprocessor, Pentium processor	Example: 8051, 8052 microcontroller
S.No	Microprocessor	Microcontroller																								
1	It is just a CPU i.e. central processing unit with address and data bus. It requires memory and other peripherals to make a computer	It is a computer on single chip. It consists of CPU memory and peripherals in a single chip.																								
2	It does not have digital input output ports. Needs to be externally connected	It has several digital input output lines 8051 has 32 I/O lines																								
3	It is mainly used for information processing, multimedia and for making desktop computer.	It is mainly used for digital control in industrial applications or in home appliances																								
4	It can have large external memory	Memory capacity is small																								
5	It is based on VonNeumann architecture	It is based on Harward architecture																								
6	Cost and size of hardware is large	It is cheaper in cost and compact in size																								
7	Example: 8085 microprocessor, Pentium processor	Example: 8051, 8052 microcontroller																								




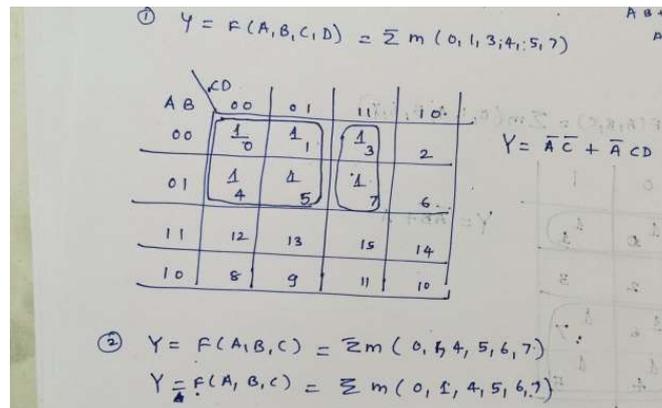c) Solve the following SOP expressions with the help of K-map :
(i) $F(A, B, C, D) = \sum m (0, 1, 3, 4, 5, 7)$ (ii) $F(A, B, C) = \sum m (0, 1, 4, 5, 6, 7)$

Ans: (i) $F(A, B, C, D) = \sum m (0, 1, 3, 4, 5, 7)$: (2 Mark)



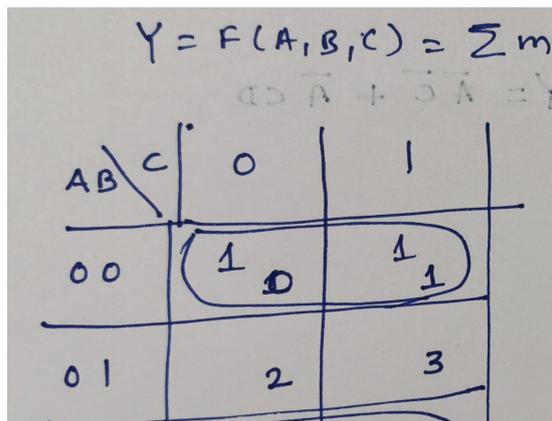(ii) $F(A, B, C) = \sum m (0, 1, 4, 5, 6, 7)$: (2 Mark)



d) Write any two laws of Boolean algebra. Justify with the help of truth table.

Ans: (4 Marks)

The basic Laws of Boolean Algebra can be stated as follows: (Any Two expected)

1. **Commutative Law** states that the interchanging of the order of operands in a Boolean equation does not change its result. For example:
 1. OR operator $\rightarrow A + B = B + A$
 2. AND operator $\rightarrow A * B = B * A$
2. **Associative Law** of multiplication states that the AND operation are done on two or more than two variables. For example:
 $A * (B * C) = (A * B) * C$
3. **Distributive Law** states that the multiplication of two variables and adding the result with a variable will result in the same value as multiplication of addition of




the variable with individual variables. For example:
 $A + BC = (A + B) (A + C)$.

OR

1. Annulment law:
 $A \cdot 0 = 0$
 $A + 1 = 1$
2. Identity law:
 $A \cdot 1 = A$
 $A + 0 = A$
3. Idempotent law:
 $A + A = A$
 $A \cdot A = A$
4. Complement law:
 $A + A' = 1$
 $A \cdot A' = 0$
5. Double negation law:
 $((A)')' = A$
6. Absorption law:
 $A \cdot (A+B) = A$
 $A + AB = A$

OR

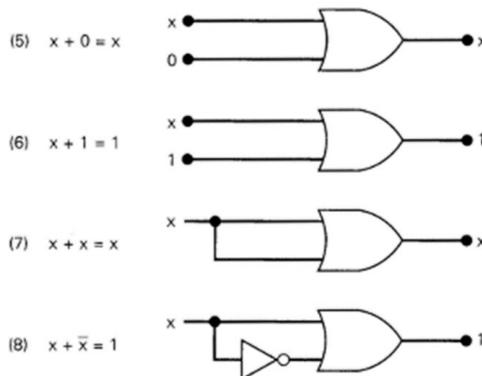

or equivalent table

Q.3	Attempt any THREE of the following	12 Marks
	a) List any eight features of microcontroller 8051.	
Ans:	Following features of microcontroller 8051.	

(Any four point expected: 1 mark each, total 4 Mark)



- 1) 4kbytes of Program memory
- 2) 128 bytes of data memory
- 3) 1 serial port
- 4) 2 internal timers of 16bit
- 5) 40 pin device
- 6) Power supply voltage 5V
- 7) 5 interrupt sources
- 8) Harward architecture
- 9) 32 bidirectional IO lines divided in 4 IO ports
- 10) 16 address and 8 data lines available on port P0 and P2

b) Compare TTL, CMOS & ECL families on the following : (i) Power dissipation (ii) Noise Margin (iii) Speed of Operation (iv) Fan-in

Ans: (Each point : 1 Mark, Total 4 Mark)

S.No	Point	TTL	CMOS	ECL
1	Power dissipation	10mW	0.001mW	175mW
2	Noise margin	Very good 0.5V	Excellent, 1.5V	Good 0.16V
3	Speed of operation	fast	Moderate	fastest
4	Fan-in	12-14	>10	>10

c) Describe the function of following pins of 8051 : (i) PSEN (ii) RESET (iii) ALE (iv) $\bar{E}A$

Ans: PSEN- (1 Mark)

It is an output control signal used to enable external program memory. It is to be connected to /RD pin of external program memory.

RESET: (1 Mark)

It is active high input signal to 8051 used to reset 8051. When it is HIGH, 8051 program counter is reset to 0000h.



ALE:

(1 Mark)

Address latch enable. It is output control signal to indicate presence of address on lower 8 bit address lines AD0-AD7 on port P0.

$\bar{E}A$ -


(1 Mark)

It is active low control input signal. When $\bar{E}A$ is at logic 0, external program memory is used. When $\bar{E}A$ is at logic 1, internal program memory is used for address range 0000-0FFF.


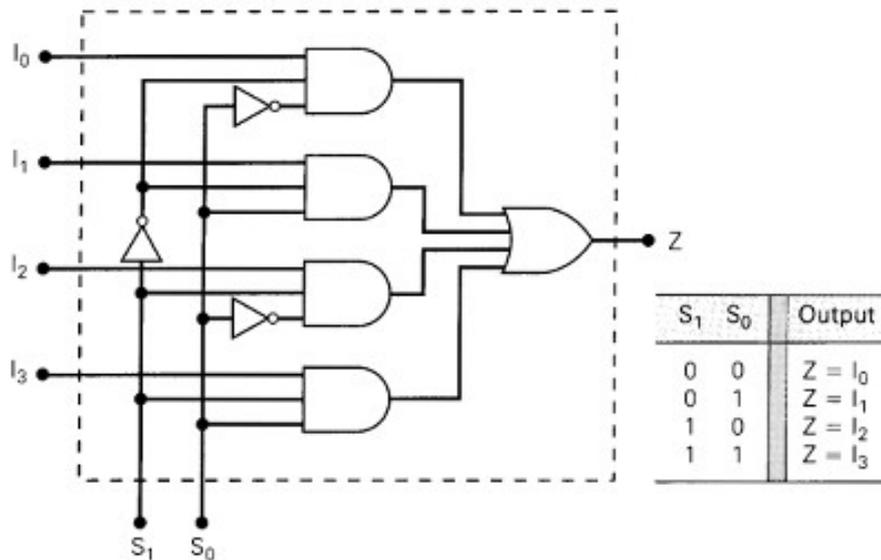
d) Draw logic diagram of 4 : 1 multiplexer & give it's truth table.

Ans: logic diagram of 4 : 1 multiplexer & give it's truth table :

(Diagram: 2 Mark, Truth table: 2 Mark, Total 4 Mark)



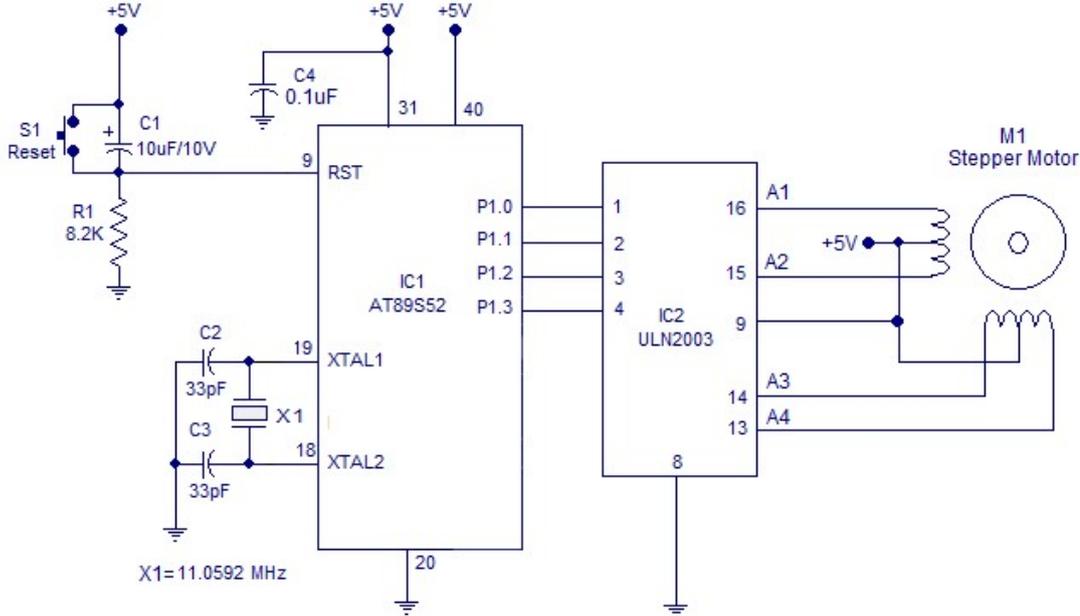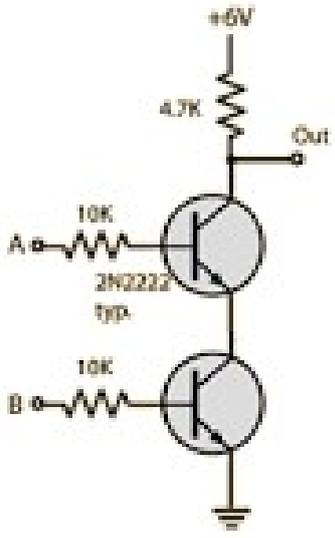

Q.4	Attempt any THREE of the following	12 Marks
a)	Draw a neat labelled interfacing diagram of 8051 with stepper motor.	
Ans:	labelled interfacing diagram of 8051 with stepper motor: 	(4 Mark)
b)	Implement OR gate using transistor.	
Ans:	OR gate using transistor: 	(4 Mark)

or equivalent figure

or equivalent figure



c) Write the alternative function of Port-3 pins.

Ans: Alternative function of Port-3 pins:


(4 Marks)

Port Pin	Alternate Function
P3.0	RXD (serial input port)
P3.1	TXD (serial output port)
P3.2	$\overline{\text{INT0}}$ (external interrupt 0)
P3.3	$\overline{\text{INT1}}$ (external interrupt 1)
P3.4	T0 (Timer 0 external input)
P3.5	T1 (Timer 1 external input)
P3.6	$\overline{\text{WR}}$ (external data memory write strobe)
P3.7	$\overline{\text{RD}}$ (external data memory read strobe)

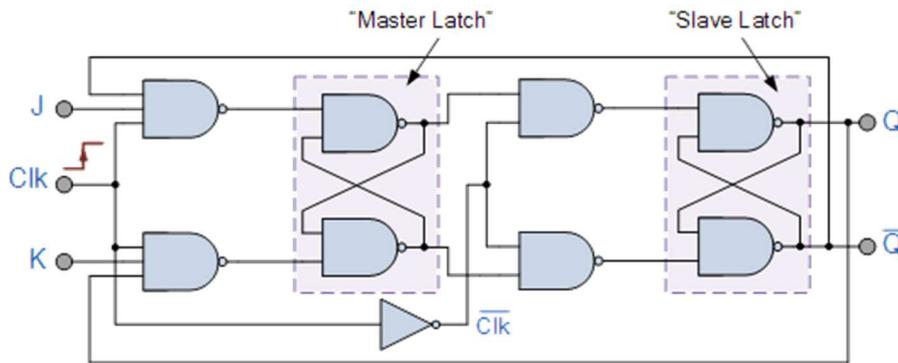d) Draw master-slave JK FF & write it's truth table.

Ans: Master-slave JK FF & write it's truth table:

(Diagram: 2 Mark & truth table : 2 Marks)



or equivalent figure

J	K	CLK	Q	Q'	
0	0		Q ₀	Q ₀ '	Hold
0	1		0	1	Reset
1	0		1	0	Set
1	1		Q ₀ '	Q ₀	Toggle (opposite state)

e) Explain Boolean processor of 8051.

Ans: Explanation: Boolean processor of 8051:

(4 Marks)

The Boolean processor of 8051 offers single bit operations.
 The internal RAM contains 128 bit addressable bits.



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION
(Autonomous)
(ISO/IEC-27001-2005 Certified)

SUMMER– 2019 Examinations

Subject Code: 22421

Model Answer

Page 10 of 13

All port lines are bit addressable
Many SFRs are bit addressable. E.g. Accumulator, PSW register, TCON, IE register.
Different Boolean instructions are


Mnemonic		Description	Byte	Cyc
SETB	C	Set Carry flag	1	1
SETB	bit	Set direct Bit	2	1
CLR	C	Clear Carry flag	1	1
CLR	bit	Clear direct bit	2	1
CPL	C	Complement Carry flag	1	1
CPL	bit	Complement direct bit	2	1
MOV	C.bit	Move direct bit to Carry flag	2	1
MOV	bit.C	Move Carry flag to direct bit	2	2
ANL	C.bit	AND direct bit to Carry flag	2	2
ANL	C.bit	AND complement of direct bit to Carry flag	2	2
ORL	C.bit	OR direct bit to Carry flag	2	2
ORL	C.bit	OR complement of direct bit to Carry flag	2	2
JC	rel	Jump if Carry is flag is set	2	2
JNC	rel	Jump if No Carry flag	2	2
JB	bit.rel	Jump if direct Bit set	3	2
JNB	bit.rel	Jump if direct Bit Not set	3	2
JBC	bit.rel	Jump if direct Bit is set & Clear bit	3	2

Q.5 Attempt any TWO of the following 12 Marks

a) Execute the following program & specify the contents of Accumulator & status of PSW after execution. Also draw the format of PSW
MoV A, #0FH
MoV B, #03H
Div AB
End

Ans: (6 Marks)

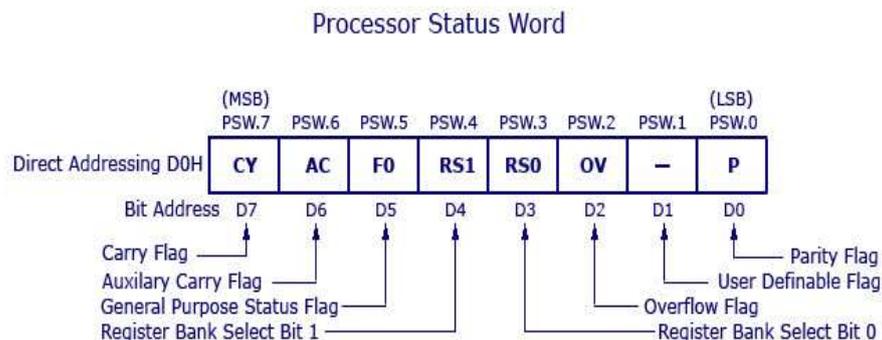- 1) ACC will be loaded with number 0Fh (15 decimal)
- 2) B register will be loaded with 03h (03 decimal)
- 3) Division instruction will be executed
- 4) Contents of A = 05H , B= 00h,
Carry flag =0, OV flag =0





b) Develop an ALP to generate square wave of 1kHz at port pin P1.3. Draw flowchart for it.

Ans:

(6 Marks)

```

//assume clock input 12Mhz
//required counts = 65536-500=FE0Ch
MOV P1,#00000000B
MOV TMOD,#00000001B
MAIN:  SETB P1.0
       ACALL DELAY
       CLR P1.0
       ACALL DELAY
       SJMP MAIN

DELAY:  MOV TH0,#0FEH
       MOV TL0,#00CH
       SETB TR0
HERE:   JNB TF0,HERE
       CLR TR0
       CLR TF0
       RET
       END

```


A suitable flow chart may be given credit.

c) Explain full adder with it's logic diagram & truth table.

Ans:

full adder with it's logic diagram & truth table:

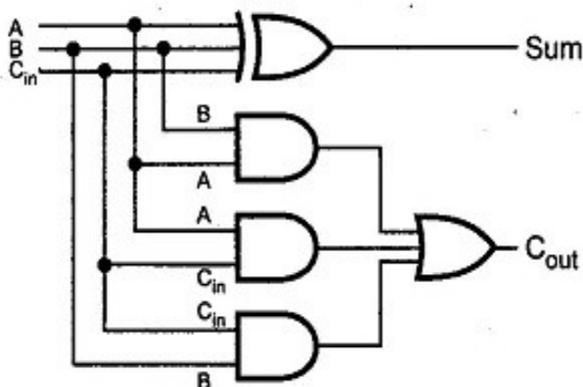(Diagram: 3 Mark & Truth table: 3 Mark, Total 6 Marks)



Inputs			Outputs	
A	B	C _{in}	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

or equivalent figure



Q.6	Attempt any TWO of the following	12 Marks
a)	Construct 3-bit synchronous UP counter using flip-flop. Also draw it's timing diagram.	
Ans:	3-bit synchronous UP counter using flip-flop :	(3 Marks)
	<p style="text-align: center;">or Equivalent diagram</p>	
	Timing diagram:	(3 Marks)
	<p style="text-align: center;">or Equivalent diagram</p>	
b)	Describe the following assembler directives with one example of each : (i) ORG (ii) DB (iii) EQU (iv) END (v) CODE (vi) DATA	
Ans:	(Each assembler directives : 1 Mark, Total 6 Marks)	
	<p>i) ORG: (Origin) It is the assembler directive to indicate starting address of program. Example: ORG 0000h LJMP MAIN</p> <p>ii) DB – Define Byte It is the directive used to define 8 bit data example: DATA1 DB 39H</p>	

22421

11920

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Sketch symbol and write truth table of two input EX-OR gate.
- (b) Define the term 'Multiplexer'. State two examples of multiplexer.
- (c) Implement T flip flop using J K flip flop. Write its truth table.
- (d) Implement following Boolean equation using fundamental gates :
$$Y = ABC + A\bar{B}C + \bar{A}\bar{C}B$$
- (e) Identify direct addressing instructions from following instructions :
 - (i) MOV R0, R5
 - (ii) MOV R0, 80 H
 - (iii) MOV R0, #75H
 - (iv) ADD A, 45 H

[1 of 4]

P.T.O.

- (f) If initial content of accumulator is 44 H, find out the new content of accumulator after execution of the instruction

RR A

- (g) Find out number of data lines required to interface 16 LEDs arrange in the 4×4 matrix form.

2. Attempt any THREE of the following :

12

- (a) Define following terms related to logic families :
- (i) Noise Margin
 - (ii) FAN-OUT
 - (iii) Propagation delay
 - (iv) Power dissipation
- (b) State Demorgan's theorem's and prove both theorems using truth table.
- (c) State functions of preset, clear, clock and SR inputs related to SR flip flop.
- (d) Sketch diagram of 4 bit asynchronous counter using suitable flip flop. Sketch timing diagram.

3. Attempt any THREE of the following :

12

- (a) List out any four assembler directives and state their functions.
- (b) Sketch diagram showing interfacing of two chips of RAM having size $2k \times 8$ to 8051 microcontroller. Write its memory map.
- (c) Minimize following Boolean equation using 'k' map :
- $$Y = A \bar{B} C + \bar{A} \bar{B} C + \bar{A} \bar{B} \bar{C} + ABC$$
- and implement using basic gates.
- (d) List out three types of buses. State their functions.

- 4. Attempt any THREE of the following :** **12**
- (a) List out features of any four addressing modes of 8051.
 - (b) With the help of PCON register, explain Power down mode and Idle mode of 8051.
 - (c) Construct full adder circuit using K map.
 - (d) Justify 'NOR gate is called as universal gate'. Sketch relevant diagram.
 - (e) Compare microprocessor with microcontroller on the basis of any four factors.
- 5. Attempt any TWO of the following :** **12**
- (a) Explain with neat diagram microcontroller based water level controller.
 - (b) Develop ALP for 8051 to perform addition, anding, multiplication of two data – Data-1 is at memory location 55 H and Data 2 is 20 H. Store result at internal memory locations.
 - (c) Explain internal and external memory organisation of 8051.
- 6. Attempt any TWO of the following :** **12**
- (a) Explain functions of all pins of Port 0, Port 1, Port 2 and Port 3.
 - (b) Sketch diagram showing interfacing of single 7-segment common Anode display to 8051. Develop ALP to display number '7,' on it.
 - (c) Convert following Boolean equation to standard SOP form and implement using NAND-NAND logic.
 - (i) $y = A \bar{B} C + ABC \bar{D} + A \bar{C} D$
 - (ii) $y = PQ + PQR + PQ \bar{R}$
-



Important suggestions to examiners:


- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance. (Not applicable for subject English and communication skills)
- 4) While assessing figures, examiner may give credit for principle components indicated in a figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case some questions credit may be given by judgment on part of examiner of relevant answer based on candidate understands.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q.1	Attempt any FIVE of the following	10 Marks															
a)	Sketch symbol and write truth table of two input EX-OR gate.																
Ans:	1 mark for diagram and 1 for TT																
	 $x = A \oplus B$ $= \bar{A}B + A\bar{B}$	<table border="1" data-bbox="1197 1366 1412 1579"><thead><tr><th>A</th><th>B</th><th>x</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	0
A	B	x															
0	0	0															
0	1	1															
1	0	1															
1	1	0															
b)	Define the term 'Multiplexer'. State two examples of multiplexer.																
Ans:	1 mark for definition and 1 for types																
	A digital multiplexer or data selector is a logic circuit that accepts several (many) digital data inputs and selects one of them at any given time to pass on to the output. 1. Two input multiplexer 2. Four input multiplexer 3. Eight input multiplexer																
c)	Implement T flip flop using J K flip flop. Write its truth table.																
Ans:																	




1 mark for Truth table and 1 for diagram

T flip-flop input	Present State	Next State
T	Q _t	Q _{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

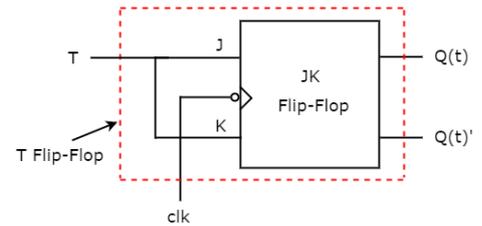

d) Implement following Boolean equation using fundamental gates : $Y = ABC + A\bar{B}C + \bar{A}\bar{C}B$

Ans:

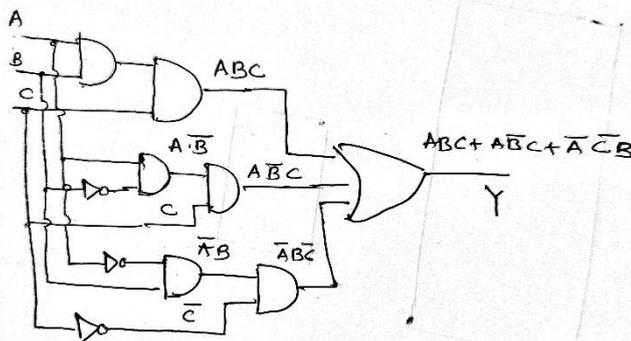

2 marks for correct diagram

e) Identify direct addressing instructions from following instructions :

(i) MOV RO, R5 (ii) MOV RO, 80 H (iii) MOV RO, #75H (iv) ADD A, 45 H

Ans: Instructions ii) and iv) are direct addressing as 80H and 45H are direct addresses **2marks**

f) If initial content of accumulator is 44 H, find out the new content of accumulator after execution of the instruction RR A

Ans: Contents of Acc will be 22H (as RR A divides acc by 2) **2 marks**

g) Find out number of data lines required to interface 16 LEDs arrange in the 4 x 4 matrix form.

Ans: 4+4=8, eight lines are required for 4x4 matrix of 16 LEDs **2 marks**

Q. 2 Attempt any THREE of the following 12 Marks

a) Define following terms related to logic families :

(i) Noise Margin (ii) FAN-OUT (iii) Propagation delay (iv) Power dissipation

Ans: **1 marks for each definition**

i) Noise immunity is measured in terms of **noise margin**.

High state Noise margin = $V_{NH} = V_{OH(min)} - V_{IH(min)}$

Low state Noise margin = $V_{NL} = V_{IL(max)} - V_{OL(max)}$



WINTER- 2019 Examinations

Subject Code: 22421

Model Answer

Page 3 of 15


	<p>i) The fan-out is defined as the maximum number of logic inputs that an output can Drive reliably.</p> <p>ii) Propagation delay is defined as t_{PLH} Delay time in going from logical 0 to logical 1 state (LOW to HIGH) t_{PHL} Delay time in going from logical 1 to logical 0 state (HIGH to LOW)</p> <p>iii) Average power dissipation is defined as $PD_{(avg)} = ICC_{(avg)} * V_{CC}$</p>
b)	State Demorgan's theorem's and prove both theorems using truth table.
Ans:	<p style="color: red;">2 marks for statement and 2 marks for equation</p> <p>De Morgan's 1st theorem states that when the OR sum of two variables is inverted, this is the same as inverting each variable individually and then ANDing these inverted variables.</p> <p>De Morgan's 2nd theorem says that when the AND product of two variables is inverted, this is the same as inverting each variable individually and then ORing them.</p> <p>In Boolean equation form it can be written as</p> $\overline{(x + y)} = \bar{x} \cdot \bar{y}$ $\overline{(x \cdot y)} = \bar{x} + \bar{y}$
c)	State functions of preset, clear, clock and SR inputs related to SR flip flop.
Ans:	<p style="color: red;">1 mark each for each function</p> <p>Preset Input: is an asynchronous input to set the Q output to 1</p> <p>Clear Input: is also asynchronous input to reset the Q output to 0</p> <p>Clock Input: is used to input external logic clock pulse (HIGH-LO) to the flip-flop. Depending upon the status of the input signal Q output changes on each clock pulse transition (Lo-Hi, Hi-Lo)</p> <p>SR input: The S input is Set input that is used to set the Q output. And R is the reset input which is used to reset Q output of the flipflop.</p>
d)	Sketch diagram of 4 bit asynchronous counter using suitable flip flop. Sketch timing diagram.
Ans:	<p style="color: red;">2 marks for diagram and 2 for timing diagram</p> <div style="text-align: center;"> </div> <p style="text-align: center; font-size: small;">*All J and K inputs assumed to be 1.</p>



Q.3	Attempt any THREE of the following 12 Marks
a)	List out any four assembler directives and state their functions.
Ans:	1 marks for each directive ORG directive: It is used to specify starting address of the Program. A 16bit address follows ORG ORG 0020H will start program from 0020H memory location. END directive: It indicates end of the assembly language program DB directive: he DB directive is the most widely used data directive in the assembler. It is used to define the 8-bit data. When DB is used to define data, the numbers can be in decimal, binary, hex, or ASCII formats. EQU directive: This is used to define a constant without occupying a memory location. The EQU directive does not set aside storage for a data item but associates a constant value with a data label so that when the label appears in the program, itp constant value will be substituted for the label.
b)	Sketch diagram showing interfacing of two chips of RAM having size 2k x 8 to 8051 microcontroller. Write its memory map.
Ans:	




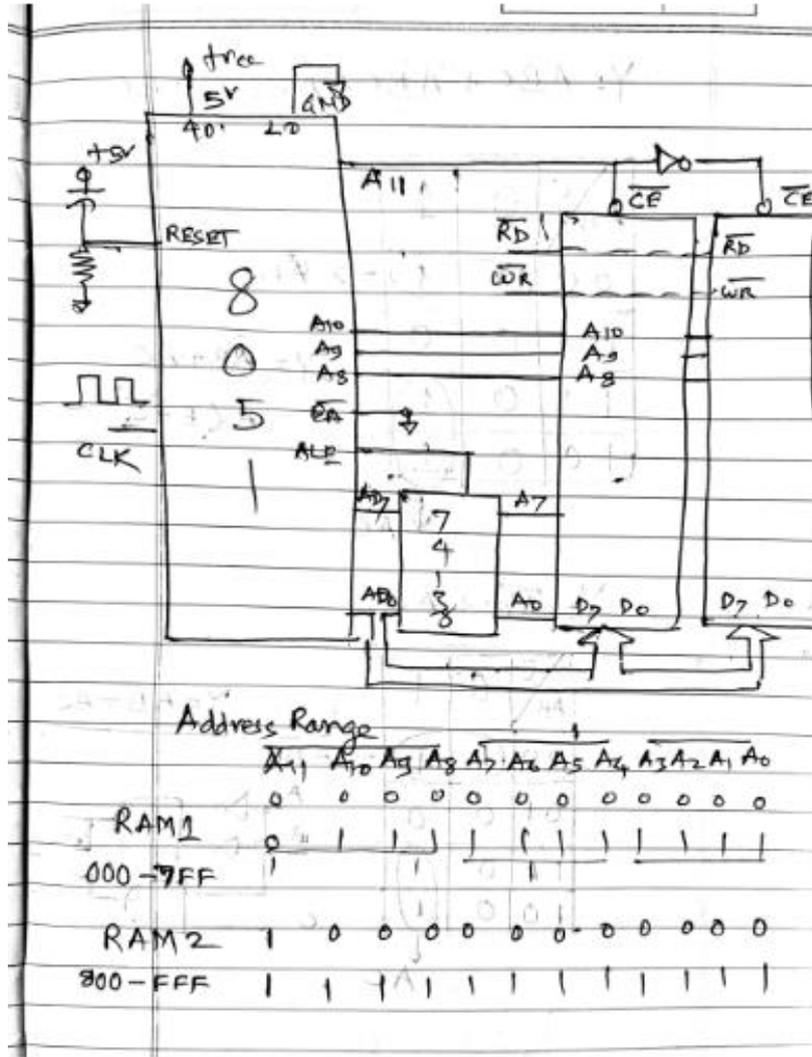3 marks for diagram and 1 mark for address range



c) Minimize following Boolean equation using 'K' map : $Y = A\bar{B}C + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC$ and implement using basic gates.

Ans: 2 mark for k map 2 mark for diagram

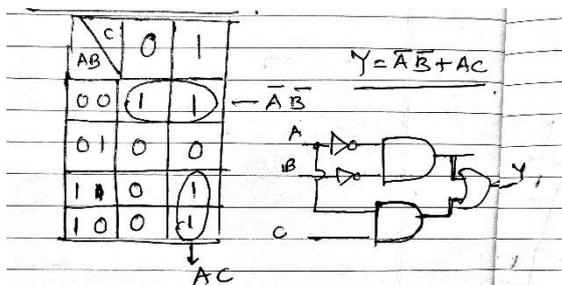

d) List out three types of buses. State their functions.



	1 for address bus 1 for data bus and 2 for control bus																		
Ans:	<p>1. Address Bus: It is a group of lines which carry binary address of the peripheral to be interface.</p> <p>2. Data Bus: It is used to Read/Write to between CPU and the peripheral</p> <p>3. Control Bus: This is a group of lines that generates control signals e.g. RD, WR, CLOCKOUT etc.</p>																		
Q.4	12 Marks																		
a)	List out features of any four addressing modes of 8051.																		
Ans:	<p style="text-align: center;">1.5 marks for each address modes</p> <p>1. Immediate addressing mode: In this Immediate Addressing Mode, the data is provided in the instruction itself. The data is provided immediately after the opcode. These are some examples of Immediate Addressing Mode. MOVA, #0AFH;</p> <p>2. Register addressing mode: In the register addressing mode the source or destination data should be present in a register (R0 to R7). These are some examples of Register Addressing Mode. MOVA, R5; MOVR0, A;</p> <p>3. Direct Addressing Mode: In the Direct Addressing Mode, the source or destination address is specified by using 8-bit data in the instruction. Only the internal data memory can be used in this mode. Here some of the examples of direct Addressing Mode. MOV80H, R6; MOVR2, 45H; MOVR0, 05H;</p> <p>4. Register indirect addressing Mode: In this mode, the source or destination address is given in the register. By using register indirect addressing mode, the internal or external addresses can be accessed. The R0 and R1 are used for 8-bit addresses, and DPTR is used for 16-bit addresses, no other registers can be used for addressing purposes. Let us see some examples of this mode. MOV 0E5H, @R0 MOV @R1, 80H</p>																		
b)	With the help of PCON register, explain Power down mode and Idle mode of 8051.																		
Ans:	<p style="text-align: center;">2 marks for PCON format and 2 marks for explanation</p> <p>The format for PCON register is as follows</p> <table style="margin-left: auto; margin-right: auto; border-collapse: collapse;"> <tr> <td style="text-align: center;">7</td> <td style="text-align: center;">6</td> <td style="text-align: center;">5</td> <td style="text-align: center;">4</td> <td style="text-align: center;">3</td> <td style="text-align: center;">2</td> <td style="text-align: center;">1</td> <td style="text-align: center;">0</td> <td></td> </tr> <tr> <td style="text-align: center; border: 1px solid black;">SMOD</td> <td style="text-align: center; border: 1px solid black;">---</td> <td style="text-align: center; border: 1px solid black;">---</td> <td style="text-align: center; border: 1px solid black;">---</td> <td style="text-align: center; border: 1px solid black;">GF1</td> <td style="text-align: center; border: 1px solid black;">GF0</td> <td style="text-align: center; border: 1px solid black;">PD</td> <td style="text-align: center; border: 1px solid black;">IDL</td> <td style="text-align: right; padding-left: 5px;">PCON</td> </tr> </table> <p>Bit 7 - SMOD 1 = Baud rate is doubled in UART mode 1, 2 and 3. 0 = No effect on Baud rate.</p>	7	6	5	4	3	2	1	0		SMOD	---	---	---	GF1	GF0	PD	IDL	PCON
7	6	5	4	3	2	1	0												
SMOD	---	---	---	GF1	GF0	PD	IDL	PCON											



Bit 3:2 - GF1 & GF0:

These are general purpose bit for user.

Bit 1 - PD: Power Down

1 = Enable Power Down mode. In this mode, Oscillator clock turned OFF and both CPU and peripherals clock stopped. Hardware reset can cancel this mode.

0 = Disable Power down mode.

Bit 0 - IDL: Idle

1 = Enable Idle mode. CPU clock turned off whereas internal peripheral module such as timer, serial port, interrupts works normally. Interrupt and H/W reset can cancel this mode.

0 = Disable Idle mode.

Power down and Idle mode features are used to save power in microcontrollers. 8051 has inbuilt power saving feature which is useful in embedded applications where power consumption is main constraint. In **Power Down** mode, the oscillator clock provided to system is OFF i.e. CPU and peripherals clock remains inactive in this mode.

In **Idle** Mode, only the clock provided to CPU gets deactivated, whereas peripherals clock will remain active in this mode.


Hence power saved in power down mode is more than in idle mode.

c) Construct full adder circuit using K map.


Ans: 2 marks for k map, 2 marks for description, 2marks for diagram

Inputs			Carry	Sum
x	y	p	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table

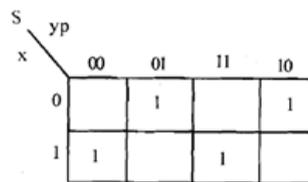

(b) K-Map for 'S'

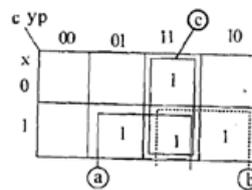


(c) K - Maps for 'C'

There are three inputs to full adder x,y and previous carry bit p. The truth table shows the all possible combinations and the results of addition Sum (s)and Carry (c). the K-map for both sum and carry are shown on right. The Boolean equations are as follows

$$C = x p + x y + y p$$

$$S = x \bar{y} \bar{p} + x \bar{y} p + x y \bar{p} + x y p$$

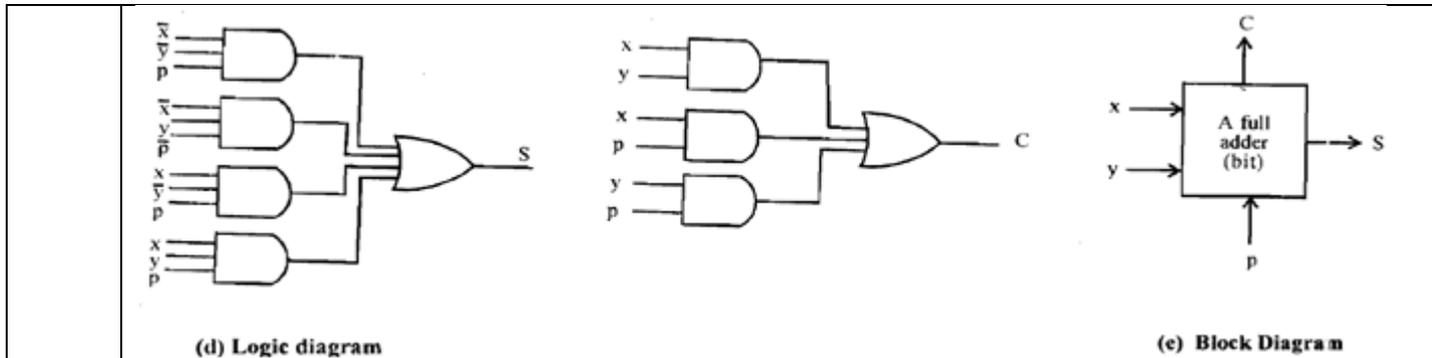
The logic circuit is shown in following diagram



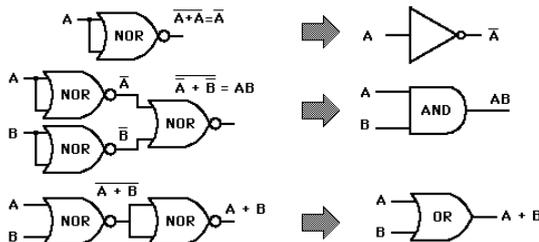d) Justify 'NOR gate is called as universal gate'. Sketch relevant diagram.

Ans: **2 marks for explanation and 4 marks for diagram**

NOR gate is universal gate which means that NOR gate can be used to construct any of the basic logic gates which is shown in the following diagram. From which it is clear that NOR gate is called as universal gate.



e) Compare microprocessor with microcontroller on the basis of any four factors.

Ans: **1.5 marks for each comparison**

	Microprocessors	Microcontrollers
1	It is only a general purpose computer CPU	It is a micro computer itself
2	Memory, I/O ports, timers, interrupts are not available inside the chip	All are integrated inside the microcontroller chip
3	This must have many additional digital components to perform its operation	Can function as a micro computer without any additional components.
4	Systems become bulkier and expensive.	Make the system simple, economic and compact
5	Not capable for handling Boolean functions	Handling Boolean functions
6	Higher accessing time required	Low accessing time
7	Very few pins are programmable	Most of the pins are programmable
8	Very few number of bit handling instructions	Many bit handling instructions
9	Widely Used in modern PC and laptops	widely in small control systems
E.g.	INTEL 8086, INTEL Pentium series	INTEL 8051, 89960, PIC16F877



Q.5	Attempt any TWO of the following	12 Marks
a)	Explain with neat diagram microcontroller based water level controller. 4 marks for diagram and 2 marks for explanation	
Ans:	<p>This water level controller monitors the level of the over head tank and automatically switches on the water pump when ever the level goes below a preset limit. The level of the over head tank is indicated using 5 leds and the pump is switched of when the over head tank is filled. The pump is not allowed to start if the water level in the sump tank is low and also the pump is switched off when the level inside the sump tank goes low during a pumping cycle. The circuit diagram of the water level controller is shown below.</p> <p>The level sensor probes for the overhead tank are interfaced to the port 2 of the microcontroller through transistors. Have a look at the sensor probe arrangement for the overhead tank in Figure. A positive voltage supply probe goes to the down bottom of the tank. The probes for sensing 1/4, 1/2, 3/4 and FULL levels are placed with equal spacing one by one above the bottom positive probe. Consider the topmost (full level) probe, its other end is connected to the base of transistor Q4 through resistor R16. Whenever water rises to the full level current flows into the base of transistor Q4 which makes it ON and so its collector voltage goes low. The collector of Q4 is connected to P2.4 and a low voltage at P2.4 means the over head tank is not FULL. When water level goes below the full level probe, the base of Q2 becomes open making it OFF. Now its collector voltage</p>	



goes high and high at P2.4 means the tank is not full. The same applies to other sensor probes (3/4, 1/2, 1/4) and the microprocessor understands the current level by scanning the port pins P2.4, P2.5, P2.6 and P2.7. All these port pin are high (all sensor probes are open) means the tank is empty.

Port pin P0.5 is used to control the pump. When ever it is required start pumping, the controller makes P0.5 low which makes transistor Q6 ON which in turn activates the relay K1 that switches the pump. Also the LED d6 glows indicating the motor is ON. LED D7 is the low sump indicator. When the water level in the sump tank goes low, the controller makes P0.7 low which makes LED D7 to glow.

```
MOV P2,#11111111B // initiates P2 as sensor input
MOV P0,#11111111B // initiates P2 as the output port
MOV A,#00000000B
```

```
MAIN:ACALL SMPCK // checks the level of the sump tank
```

```
MOV A,P2 // moves the current status of P2 to A
CJNE A,#11110000B,LABEL1 // checks whether tank is full
SETB P0.1
SETB P0.2
SETB P0.3
SETB P0.4
CLR P0.0 // glows full level LED
SETB P0.5
```

```
LABEL1: MOV A,P2
```

```
CJNE A,#01110000B,LABEL2 // checks whether tank is 3/4
SETB P0.0
SETB P0.2
SETB P0.3
SETB P0.4
CLR P0.1 // glows 3/4 level LED
```

```
LABEL2: MOV A,P2
```

```
CJNE A,#00110000B,LABEL3 // checks whether tank is 1/2
SETB P0.0
SETB P0.1
SETB P0.3
SETB P0.4
CLR P0.2 // glows 1/2 level LED
```

```
LABEL3: MOV A,P2
```

```
CJNE A,#00010000B,LABEL4 // checks whether tank is 1/4
```





	<pre>SETB P0.0 SETB P0.1 SETB P0.2 SETB P0.4 CLR P0.3 // glows 1/4 level LED JB P0.6, LABEL4 CLR P0.5 // switches motor ON LABEL4: MOV A,P2 CJNE A,#00000000B, MAIN // checks whether tank is empty SETB P0.0 SETB P0.1 SETB P0.2 SETB P0.3 CLR P0.4 // glows EMPTY LED JB P0.6, MAIN // checks whether sump is low CLR P0.5 // switches motor ON SJMP MAIN SMPCK:JB P0.6,LABEL5 // checks whether sump is low SETB P0.7 // extinguishes the sump low indicator LED SJMP LABEL6 LABEL5: SETB P0.5 // switches the pump OFF CLR P0.7 // glows sump low indicator LED LABEL6: RET END</pre>
b)	Develop ALP for 8051 to perform addition, anding, multiplication of two data – Data-1 is at memory location 55 H and Data 2 is 20 H. Store result at internal memory locations.
Ans:	<p>3 marks for addition program and 3 marks for multiplication</p> <p>Assembly language program ;Subtraction program</p> <pre>ORG 0000h SJMP MAIN ORG 0030H CLR C MAIN: MOV A,55H ;LOA NO1 INTO ACC ADD A,20H ;ADD TO NUMBER 2 MOV 58H, A ; STORE RESULT</pre>



	<pre>MOV A,#00H ADDC A,#00H ; ADD CARRY MOV 59H,A HERE: SJMP HERE END ;MULTIPLICATION program ORG 0000h SJMP MAIN ORG 0030H CLR C MAIN: MOV A,55H ;LOAD NO1 INTO ACC MOV 0F0H,A MOV A,20H ;LOAD NO2 INTO 20H MUL AB MOV 58H, A ; STORE RESULT MOV A,0F0H MOV 59H,A HERE: SJMP HERE END</pre>
c)	Explain internal and external memory organization of 8051.
Ans:	<p>3 marks for internal data and 3 marks for external program memory</p> <p>There are two types of memories for present day 8051 chips</p> <ul style="list-style-type: none">a) Internal data memoryb) Internal program memory <p>The address range of internal data memory is 00h-7fh, SFRs i.e. special function registers are mapped within the address range 80-ffh and accessible by direct addressing. The internal program memory is 4kB and the address range is 000h-fffh. The internal data memory 00h-7fh is divided into three sections Register Banks(00h-1fh,4 Banks each having 8 registers R0-R7), 128 bits bit addressable memory area(20h-2fh), scratch pad memory area (30h-7fh).</p>



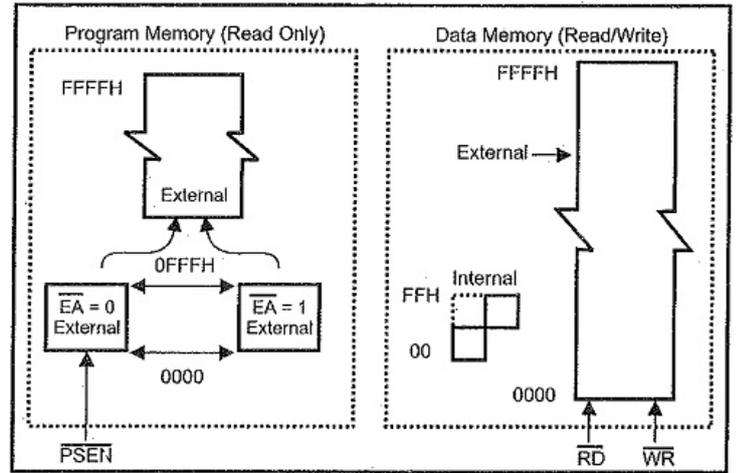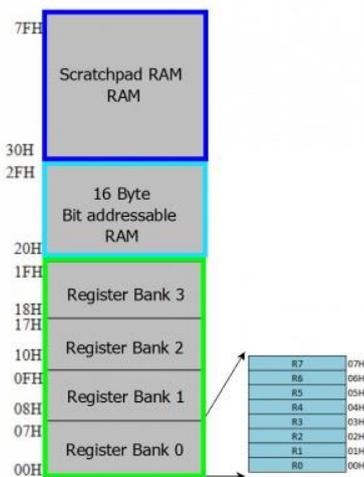The internal program memory is mapped from 000h -fffh. Its accessible when /EA pin is at logic HI, External program memory/data memory can be connected to 8051 by using its bus structure. To access external program memory /EA to be kept at logic LO. The address range of external program memory is on 64K as there are 16 address lines. The data bus is of 8 bits.



Q.6 Attempt any TWO of the following **12 Marks**

a) Explain functions of all pins of Port 0, Port 1, Port 2 and Port 3.

Ans: **4 marks for P0-P2 and 2 marks for P3**

Port 0: It has two functions. It is used as lower order multiplexed address/data bus (AD0-AD7) and it is used as general purpose I/O port. It has open collector output, it needs pullup resistance to be connected externally.

Port 1: It is only used as general purpose I/O port and it has no other function

Port 2: It has two functions. It is used as higher order address bus A8-A15. It is also used as general purpose I/O port.

Port 3: Each pin of port 3 has a different function as shown in below table. Alternatively it can also be used as general purpose I/O port.


PORT 3 ALTERNATE FUNCTIONS :

P3 BIT	FUNCTION	PIN
P3.0	RXD	10
P3.1	TXD	11
P3.2	$\overline{\text{INT0}}$	12
P3.3	$\overline{\text{INT1}}$	13
P3.4	TO	14
P3.5	TI	15
P3.6	$\overline{\text{WR}}$	16
P3.7	$\overline{\text{RD}}$	17

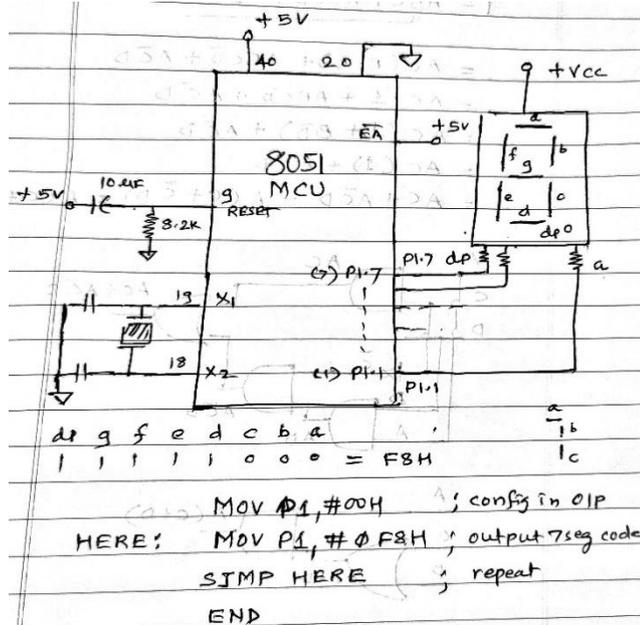b) Sketch diagram showing interfacing of single 7-segment common Anode display to 8051. Develop ALP to display number '7'; on it.



Ans: 3 marks for diagram and 3 marks for program




c) Convert following Boolean equation to standard SOP form and implement using NAND-NAND logic.

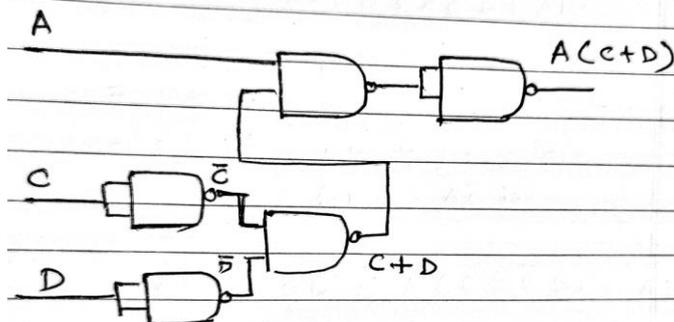(i) $y = A\bar{B}C + ABC\bar{D} + A\bar{C}D + ABC$ ii) $y = PQ + PQR + PQ\bar{R}$

Ans: 3 marks each

$$\begin{aligned}
 Y &= A\bar{B}C + ABC\bar{D} + A\bar{C}D + ABC \\
 &= AC(B + \bar{B}) + ABC\bar{D} + A\bar{C}D \\
 &= AC \cdot 1 + ABC\bar{D} + A\bar{C}D \\
 &= AC(1 + B\bar{D}) + A\bar{C}D \\
 &= AC(1) + A\bar{C}D \\
 &= AC + A\bar{C}D = A(C + \bar{C}D) = A(C + D)
 \end{aligned}$$






ii)

$$Y = PQ + PQR + PQR$$

$$= PQ(1 + R + R)$$

$$Y = PQ$$

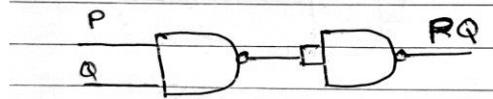

-----END-----