

22213

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) Draw symbol of:
 - (i) PN junction diode
 - (ii) LED
 - b) Name the different types of filter.
 - c) Define current gain of a transistor.
 - d) Define load and line regulation.
 - e) List any two applications of zener diode.
 - f) Draw pin configuration of IC 723.
 - g) Define Demorgans theorem first and write it's equation.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Describe the operating principle of Light Emitting Diode (LED) with neat diagram.
 - b) Draw the circuit diagram of full wave bridge rectifier and describe its working.
 - c) Describe the working of NPN transistor with a neat sketch.
 - d) Draw the block diagram of regulated power supply and state the function of each block.
- 3. Attempt any THREE of the following:** **12**
- a) Draw circuit diagram and describe the working of zener diode as voltage regulator.
 - b) Draw the circuit diagram of crystal oscillator. Give the basic principle of working of piezoelectric crystal and give the equivalent circuit diagram.
 - c) Draw the output characteristic of CE (Common Emitter) configuration and label various regions.
 - d) In full wave bridge rectifier $V_m = 10 \text{ V}$ $R_L = 10 \text{ k}\Omega$. Find out V_{DC} , I_{DC} , ripple factor and P_{IV} .
- 4. Attempt any THREE of the following:** **12**
- a) Compare positive and negative feedback (any four points).
 - b) With the help of circuit diagram and waveform, describe the working of π type filter.
 - c) For a transistor $\alpha = 0.98$ and $I_C = 4 \text{ mA}$. Calculate I_B and I_E .
 - d) Draw labelled VI characteristic of PN junction diode and explain.
 - e) Draw the circuit diagram for the following input-output waveform of rectifier (Refer Fig. No. 1 and Fig. No. 2)

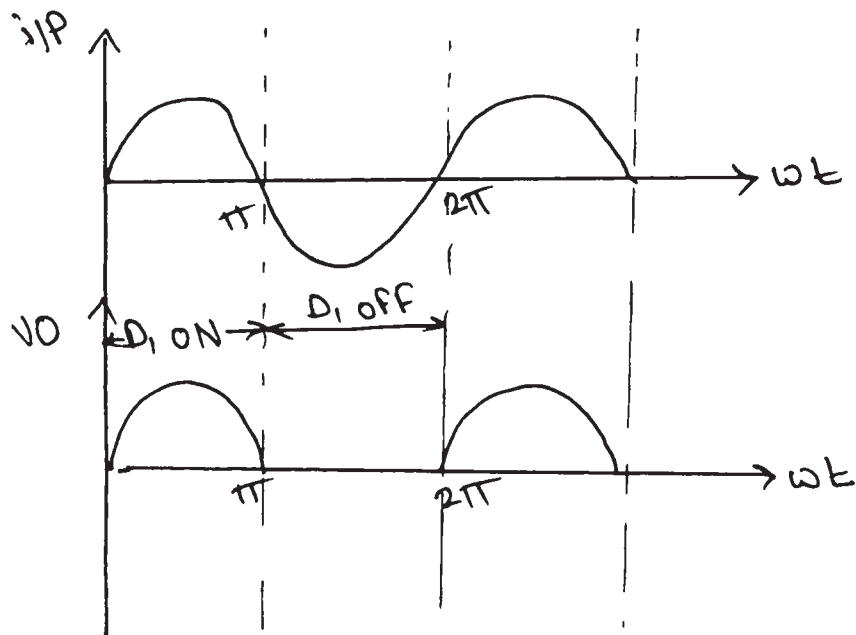


Fig. No. 1

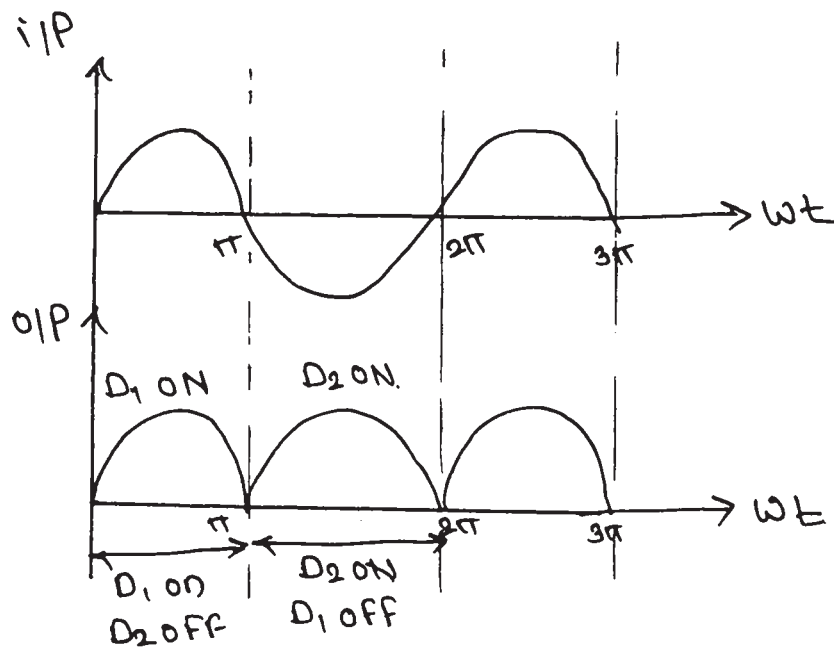


Fig. No. 2

- 5. Attempt any TWO of the following:** **12**
- a) Define α , β and γ of transistor and give the relation between α , β and γ of the transistor.
 - b) Construct a dual regulated power supply capable of giving ± 12 V using 78XX and 79XX IC's.
 - c) Define universal gate and implement NAND gate as a OR gate and EX-OR gate.
- 6. Attempt any TWO of the following:** **12**
- a) Draw RC phase shift oscillator and determine frequency of oscillation? How can the frequency of oscillator be changed.
 - b) Describe the working of transistor as a switch with a circuit diagram.
 - c) Convert:
 - (i) $(1101101)_2 = (?)_8$
 - (ii) $(513)_{10} = (?)_2$
 - (iii) $(125)_{10} = (?)_{16}$
-