

22320

12223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. **Attempt any FIVE of the following :** **10**
- a) Write radix of binary, octal, hexadecimal number system.
 - b) State necessity of demultiplexer.
 - c) Draw symbol and write the truth table for T-flipflop.
 - d) Compare between synchronous and asynchronous counter.
 - e) Write gray code to given number $(11111)_2 = (?)_{\text{Gray}}$
 - f) State two features of ADC IC0809.
 - g) Draw four variable K-map.

P.T.O.



2. Attempt any THREE of the following :

12

- a) Sketch the given Boolean expression; use one AND gate one OR gate only $Y = AB + AC$.
- b) Draw circuit diagram of BCD to seven segment decoder and write its truth table.
- c) Draw the block diagram of programmable array logic.
- d) Minimize following expression using K-map.
 $f(A,B,C,D) = \sum m(1,5,6,7,11,12,13,15)$

3. Attempt any THREE of the following :

12

- a) Realize the following logic operation using only NOR gates :
AND, OR, NOT.
- b) Describe the operation of 4 bit serial in serial out shift register.
- c) Calculate the analog output of 4 bit DAC if the digital input is 1101. Assume $V_{FS} = 5V$
- d) Describe the working of SR flipflop with its truth table and logic diagram.

4. Attempt any THREE of the following :

12

- a) Draw symbol, truth table and logical output equation of OR and EX-OR gate.
- b) Describe function of full adder circuit with its truth table and logical diagram.
- c) Design 16:1 multiplexer using 4:1 multiplexer.
- d) Describe working of Master-slave JK flipflop with truth table and logic diagram.
- e) Compare between R-2R ladder DAC and weighted resistor DAC (Four points).

5. Attempt any TWO of the following :

12

- a) Explain 3 bit asynchronous counter with output waveforms.
- b) Compare following (Any three points)
 - i) RAM with ROM memory.
 - ii) EPROM with EEPROM memory.
- c) Convert the following.
 - i) $(6AC)_{16} = (?)_{10}$
 - ii) $(2003)_{10} = (?)_{16}$
 - iii) $(228)_{10} = (?)_{BCD}$

6. Attempt any TWO of the following :

12

- a) Give the block schematic of decade counter IC 7490. Design mod-7 counter using IC.
 - b) Design a four bit BCD adder using IC-7483 and NAND gate only.
 - c) Draw the circuit and explain the principle of TTL gate with totempole output
-